
## Lab4

# 105072123 黃海茵

#### State Trasition Graph

 

IDLE: reset=1 時,回到的初始 state。

**S1:** 將 read、write 都設為 1,i 分別等於 0、1、2,經由 read\_data 讀取矩陣的 行數列數。

**S2:** 讓 i=i+1。

**MAT0**: 將 read 設為 1 ,write 設為 0 ,index 設為 0 ,經由 read\_data 讀取第一個 矩陣的資料(從第一筆開始讀)。

**MAT1**: 將 read 設為 1,write 設為 0,index 設為 1,經由 read\_data 讀取第二個 矩陣的資料(從第一筆開始讀)。

MULADD: 把兩個矩陣的兩筆資料相乘,並累加。

CHANGECOL1: 將第一個矩陣的行座標加一,直到等於行數就歸零。

WRITE: 將 read 設為 0, write 設為 1, 算出一列乘以一行的數值, 設定


write\_data 的數值,將資料寫入。

CHANGECOL2: 將第二個矩陣的行座標加一,直到等於行數就歸零。

CHANGEROW1: 將第一個矩陣的列座標加一,直到等於列數就結束運算。

## Block Diagram

(clk 跟 reset 太多了,所以用標註的)

 

## ncverilog 模擬結果

```
ncverilog 快饭高去

ncverilog: 14.10-s005: (c) Copyright 1995-2014 Cadence Design Systems, Inc. Recompiling... reason: file './MM.v' is newer than expected.
expected: Mon May 14 23:12:37 2018
actual: Mon May 14 23:18:18 2018
Caching library 'worklib' .... Done
Elaborating the design hierarchy:
Building instance overlay tables: ..... Done
Building instance overlay tables: .... Done
Building instance specific data structures.
Loading native compiled code: .... Done
Design hierarchy summary:

Instances Unique

Modules: 2
Registers: 42
Scalar wires: 6
Vectored wires: 4
Always blocks: 5
Initial blocks: 3
Cont. assignments: 1
7
***********
0 is correct.
                                                     1 is correct.
2 is correct.
                                                     3 is correct.
                                                     0 is correct.
                                                     1 is correct.
                                                     2 is correct.
3 is correct.
 Simulation complete via $finish(1) at time 9880 NS + 3
./MM tb.v:118 $finish:
```

```
ncverilog: 14.10-s005: (c) Copyright 1995-2014 Cadence Design Systems, Inc.

file: MM_syn.v

module worklib.MM_DW01_inc_0:v
errors: 0, warnings: 0

module worklib.MM_DW01_inc_1:v
errors: 0, warnings: 0

module worklib.MM_DW01_inc_2:v
errors: 0, warnings: 0

module worklib.MM_DW01_inc_3:v
errors: 0, warnings: 0

module worklib.MM_DW01_cmp6_0:v
errors: 0, warnings: 0

module worklib.MM_DW01_dec_0:v
errors: 0, warnings: 0

module worklib.MM_DW01_dec_1:v
errors: 0, warnings: 0

module worklib.MM_DW01_dec_1:v
errors: 0, warnings: 0

module worklib.MM_DW01_dec_2:v
                         errors: 0, warnings: 0
module worklib.MM_DW01_add_0:v
errors: 0, warnings: 0
module worklib.MM:v
      module worklib.MM:v
errors: 0, warnings: 0
Caching library 'worklib' ..... Done
Elaborating the design hierarchy:
Caching library 'worklib' ..... Done
ADDHXL Ul_l_18 ( A(A[18]) , .B(carry[18]) , .CO(carry[19]) , .S(SUM[18]) );
   ncelab: *E.CUVMUR (./MM_syn.v,14|15): instance 'test.mmmmm@MM<module>.add_120@MM_DW01_inc_0<module>.U1_1_18' of design unit 'ADDHXL' is unresolved in 'worklib.MM_DW01_inc_0:v'.

ADDHXL U1_1_7 ( .A(A[17]), .B(carry[17]), .CO(carry[18]), .S(SUM[17]) );
    ADDHXL DI___T ( .AKRET), .Octain ytz), .coccain tag), .Scountry) /,
reclab: *E,CUMME (./MM_syn.v,15|15): instance 'test.mmmmm@MM<module>.add_120@MM_DW01_inc_0<module>.U1_1_17' of design unit 'ADDHXL' is u
nresolved in 'worklib.MM_DW01_inc_0:v'.
ADDHXL U1_1_16 ( .A(A[16]), .B(carry[16]), .CO(carry[17]), .S(SUM[16]) );
  ncelab: *E,CUVMUR (./MM_syn.v,16|15): instance 'test.mmmmm@MM<module>.add_120@MM_DW01_inc_0<module>.U1_1_16' of design unit 'ADDHXL' is
```

這次的 lab,我在如何換行換列的部分想了很久,雖然覺得自己用了有點多 state 和 Sequential Circuits,所以導致跑得有點慢,但因為打太久所以沒時間修改了,悲慘。